



WESTERN SYDNEY
UNIVERSITY



Implementation of Leaky Integrate-and-Fire (LIF) Neurons

International Centre for Neuromorphic Systems
(ICNS)

Prerequisites:

- Basic knowledge of digital circuit design (Practical lecture 1)
- Understanding one of the Hardware design languages (Verilog or VHDL) (Practical lecture 1)
- Basic knowledge of biological neurons (Introduction to Neuroscience 800230)
- Understanding design a LIF neuron circuit using Verilog (lecture 1)


Contents:

➤ Pipeline parallel

➤ Time multiplexing

➤ **Group work:** Design a LIF neuron network using Time multiplexing and Pipeline parallel

Sequential Logic

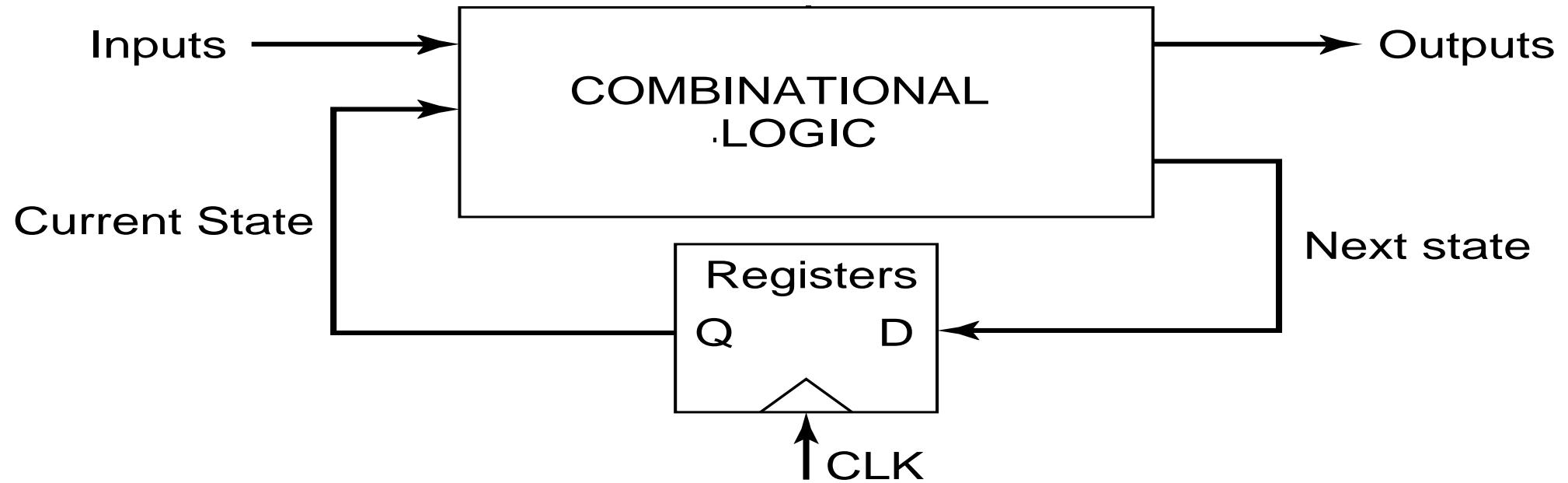


2 storage mechanisms

- positive feedback
- charge-based

Latch versus Register


❑ Latch

stores data when
clock is low

 


❑ Register

stores data when
clock rises

 

Maximum Clock Frequency

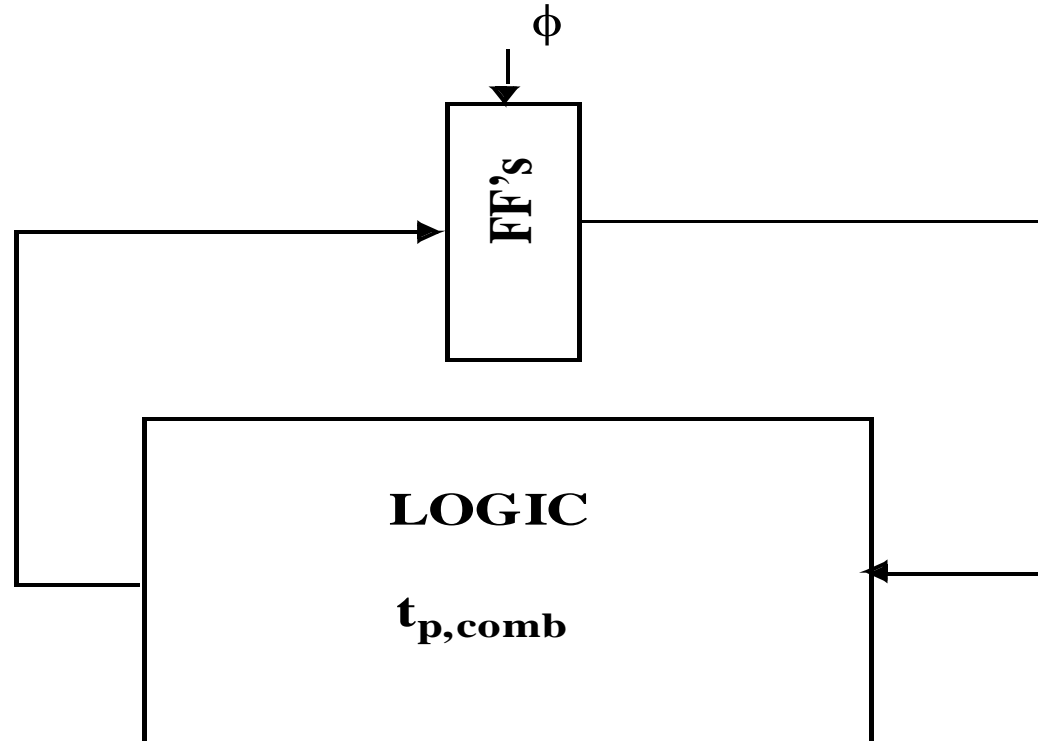


$$t_{clk-Q} + t_{p,comb} + t_{setup} = T$$

Also:



$$t_{cdreg} + t_{cdlogic} > t_{hold}$$

t_{cd} : contamination delay = minimum delay

Clk-Q Delay



 



Setup Time

  

Pipelining is Natural!

   
- Laundry Example
- Sammy, Marc, Griffy, Albert each have one load of clothes to wash, dry, and fold
- Washer takes 30 minutes
- Dryer takes 30 minutes
- “Folder” takes 30 minutes
- “Stasher” takes 30 minutes to put clothes into drawers



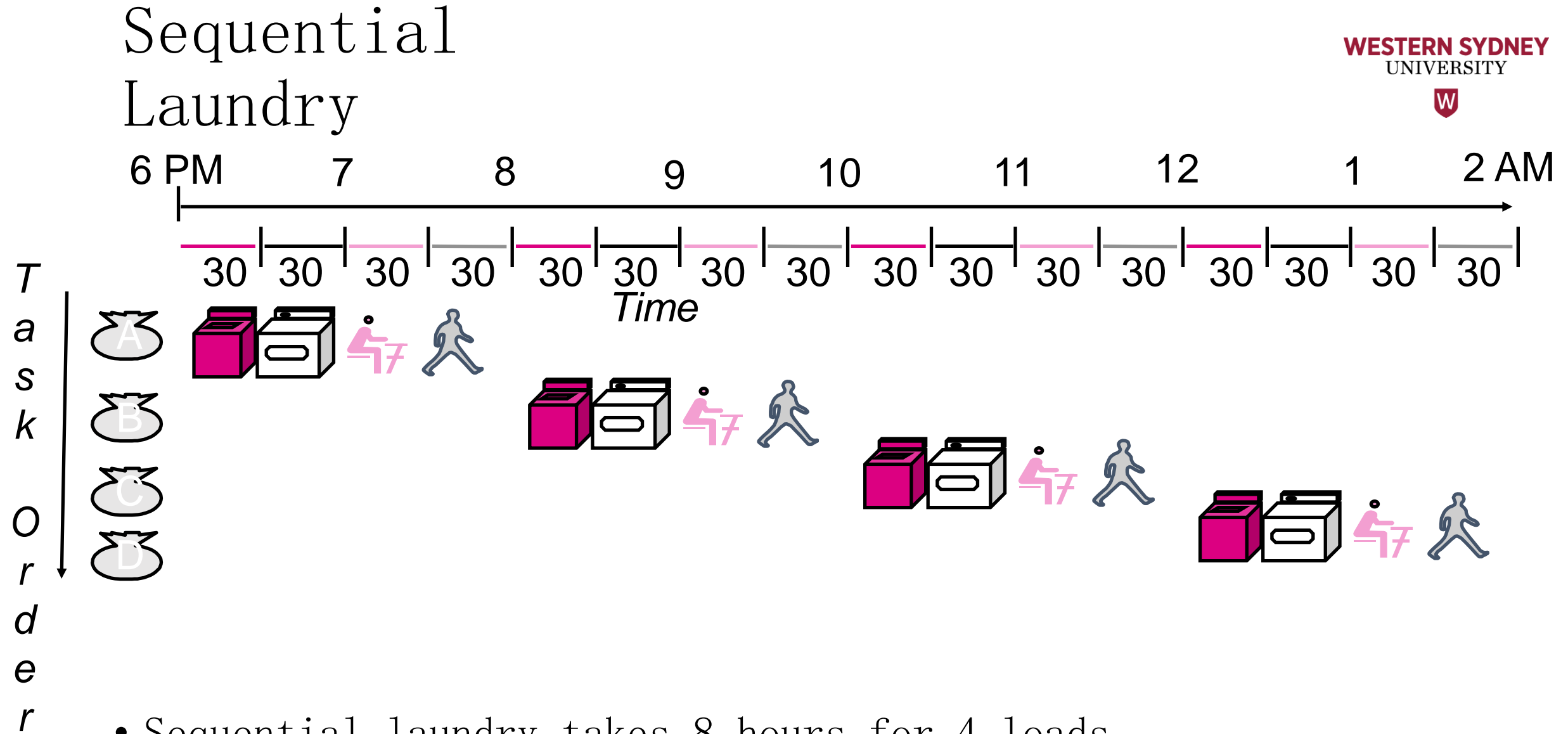


- Sequential laundry takes 8 hours for 4 loads
- If they learned pipelining, how long would laundry take?

Pipelined Laundry: Start work ASAP

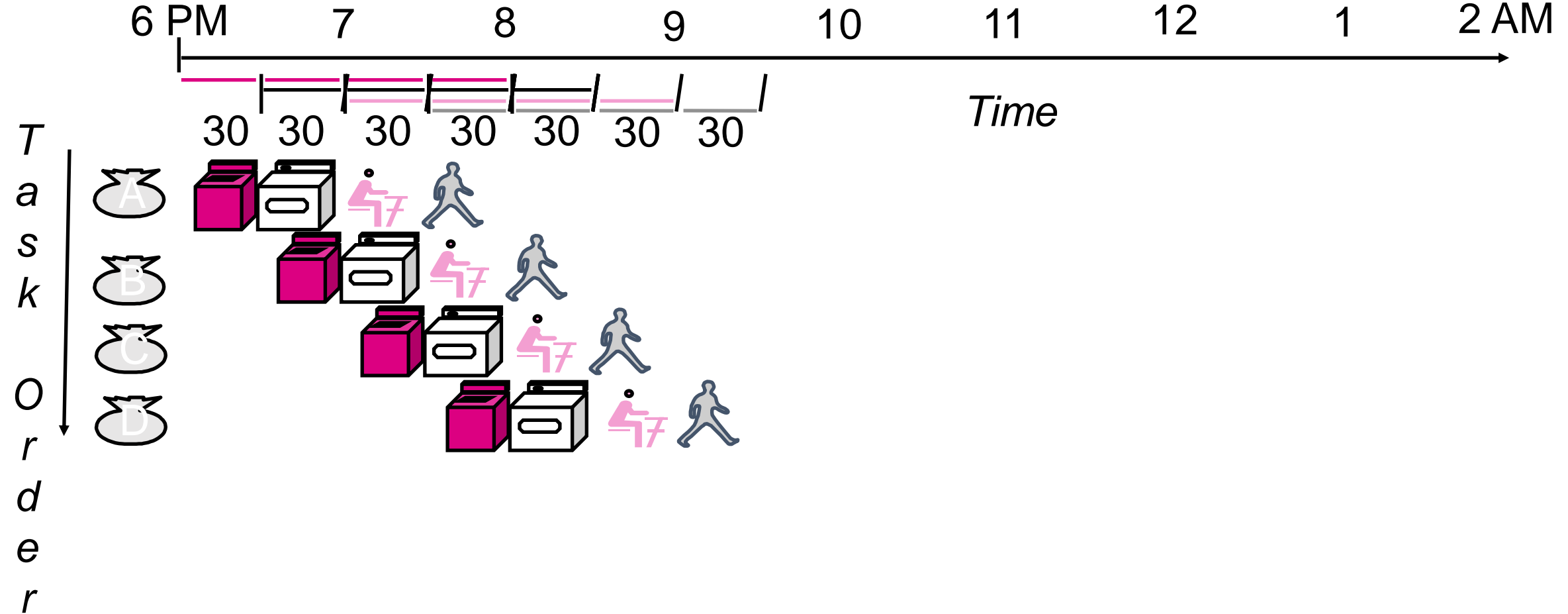

- Pipelined laundry takes 3.5 hours for 4 loads!

Pipelining Lessons

 


- Pipelining doesn't help **latency** of single task, it helps **throughput** of entire workload
- **Multiple** tasks operating simultaneously using different resources
- Potential speedup = **Number pipe stages**
- Pipeline rate limited by **slowest** pipeline stage
- Unbalanced lengths of pipe stages reduces speedup
- Time to “**fill**” pipeline and time to “**drain**” it reduces speedup
- Stall for Dependences


Why Pipeline?

- Suppose we execute 100 instructions
- Single Cycle Machine
 - $45 \text{ ns/cycle} \times 1 \text{ CPI} \times 100 \text{ inst} = 4500 \text{ ns}$
- Multicycle Machine
 - $10 \text{ ns/cycle} \times 4.6 \text{ CPI (due to inst mix)} \times 100 \text{ inst} = 4600 \text{ ns}$
- Ideal pipelined machine
 - $10 \text{ ns/cycle} \times (1 \text{ CPI} \times 100 \text{ inst} + 4 \text{ cycle drain}) = 1040 \text{ ns}$

Pipelining

 

Reference

 


Pipelined

Clock Period	Adder	Absolute Value	Logarithm
1	$a_1 + b_1$		
2	$a_2 + b_2$	$ a_1 + b_1 $	
3	$a_3 + b_3$	$ a_2 + b_2 $	$\log(a_1 + b_1)$
4	$a_4 + b_4$	$ a_3 + b_3 $	$\log(a_2 + b_2)$
5	$a_5 + b_5$	$ a_4 + b_4 $	$\log(a_3 + b_3)$

Time-multiplexing:

- FPGAs are much faster than biological neurons; a single operation on the FPGA will take only 5 nanoseconds, while a millisecond resolution is generally acceptable for neural simulations.
- Therefore, we can time-multiplex a single physical neuron to simulate many time-multiplexed (TM) neurons such that up to 200,000 TM neurons can be simulated, each one updated every millisecond.
- Using a pipelined architecture, the result of calculating one time step for a TM neuron only has to be available just before that neuron's turn comes around again. The time to compute a single neuron's output is thus not a limiting factor in the size of the network

Time-multiplexing:

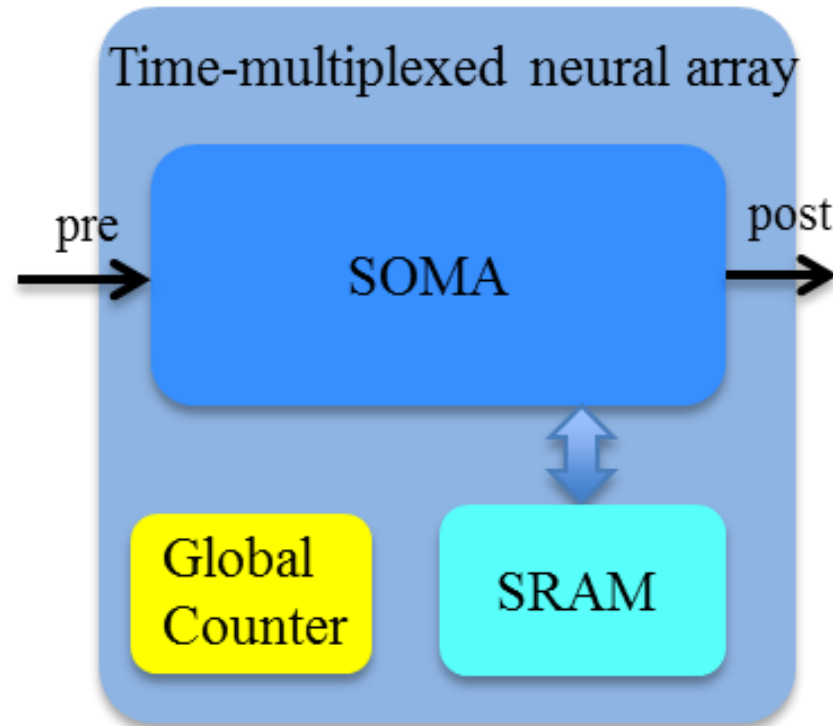

Question and discussion time

Books and publications :

Verilog and FPGA:

<https://west-sydney-primo.hosted.exlibrisgroup.com/permalink/f/afm582/UWS-ALMA2170487320001571>

Analog VLSI: Circuits and Principles:

<https://ezproxy.uws.edu.au/login?url=https://ieeexplore.ieee.org/book/6267299>

Neuromorphic silicon neuron circuits:

<https://ezproxy.uws.edu.au/login?url=https://www.frontiersin.org/articles/10.3389/fnins.2011.00073/full>

Neuromorphic engineering systems and applications:

<https://west-sydney-primo.hosted.exlibrisgroup.com/permalink/f/afm582/UWS-ALMA51173262710001571>

Summary:

- Design a pipelined LIF neuron circuit using the time-multiplexing approach
- Simulate the neuron